
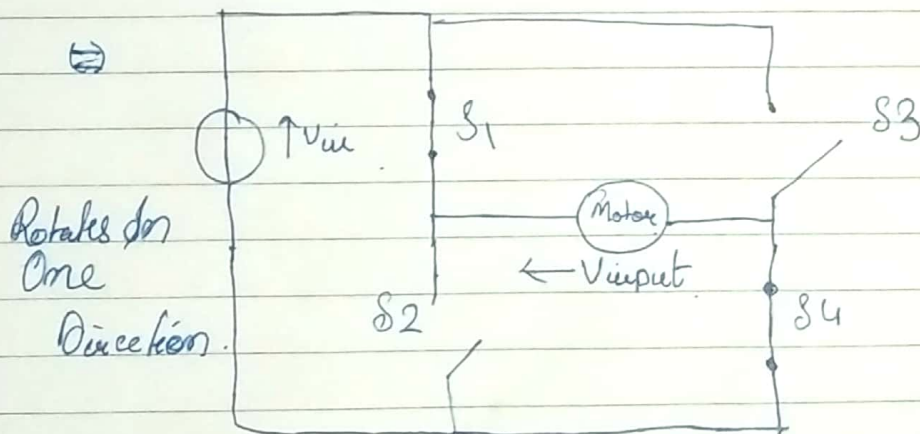


Date _____

PALLAV PANT
17BEE1092

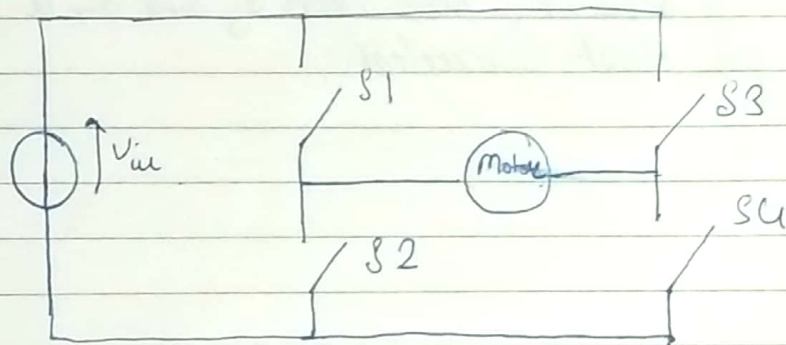
Task for Me Given By Team Technocrats

→ I have to take any number of switches and a Motor, Based upon the connection of switches, in one particular direction or other the motor will be Rotated.
↳ DC.



* → When S_1 and S_4 is closed the Motor Moves in any Particular direction.
When S_2 and S_3 is closed

Date ____ / ____ / ____

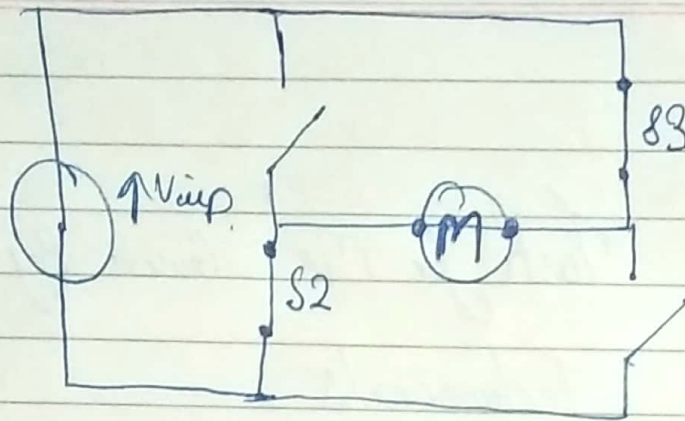

Rotates in
Another
Direction

→ When S_2 and S_3 is closed the Motor will Rotate in Any Direction.

It gets short circuited when S_1 and S_2 are closed. Also when S_3 and S_4 is closed it gets short circuited.